

GUJARAT TECHNOLOGICAL UNIVERSITY**Diploma - Semester-VI- Regular Examination May 2011****Subject code: 360908****Subject Name: Power System Operation & Control****Date: 23/05/2011****Time : 02.30 p.m. – 05.00 p.m.****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. English version is Authentic

- Q.1 (a)** Obtain the p.u. impedance diagram of the power system shown in fig A. **07**

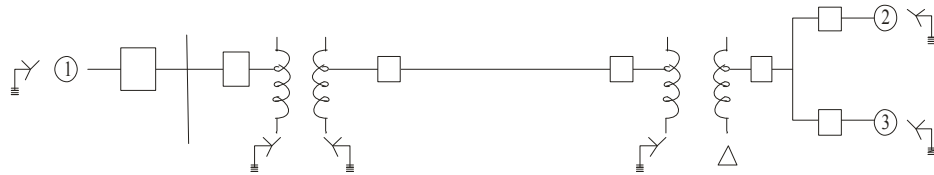


Fig A

Ge.1 30 MVA 10.5 KV $X'' = 1.6 \text{ ohm}$
 Ge.2 15 MVA 6.6 KV $X'' = 1.2 \text{ ohm}$
 Ge.3 25 MVA 6.6 KV $X'' = 0.56 \text{ ohm}$
 T1 15 MVA 33/11 KV $X = 15.2 \text{ ohm per ph on H.T. side}$
 T2 15 MVA 33/6.2 KV $X = 16 \text{ ohm per ph on H.T. side}$
 Transmission line 20.5 ohm per ph

- (b) Give single phase representation of **07**
- i) Y-Y 3 phase Transformer
 - ii) Y-Delta 3 phase Transformer
- Q.2 (a)** Explain the Gauss – siedel method to obtain the load flow solution for PQ & PV buses. **07**
- (b) Give Newton-Raphson algorithm for load flow solution for PQ buses only. **07**
- OR**
- (b) Compare fast decoupled load flow method with N-R method for obtaining load flow solution. **07**
- Q.3 (a)** What are the methods of loading turbo Generator for most economical operation. **07**
- (b) Derive the equation for economical loading of two generators at equal incremental cost neglect losses. **07**
- OR**
- Q.3 (a)** What is mean by unit commitment and what are the constraint in unit committment. **07**
- (b) Give the flow chart for unit commitment using forward Dynamic programming. **07**
- Q.4 (a)** Differentiate between single area & multi area load frequency control. **07**
- (b) Give advantages of bus admittance matrix (Y BUS) over bus Impedance matrix (Z BUS). **07**

OR

- Q.4** (a) How automatic voltage control is different from load frequency control. **07**
 (b) For the power system shown in fig B sketch the zero sequence network. **07**

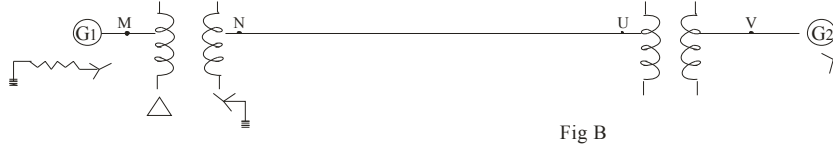


Fig B

- Q.5** (a) Prove that $M(\text{pu}) = \frac{H}{180f} S^2/\text{Elect. degree}$ for synchronous machines. **07**
 (b) Explain the term equal area criterion. **07**

OR

- Q.5** (a) What are factors affecting the transient stability. **07**
 (b) Explain the recent methods of maintaining transient stability. **07**

- પ્રશ્ન-૧** અ આકૃતિ A પરથી પાવર સિસ્ટમ નો પી. યુ. ઇમ્પિડન્સ ડાયગ્રામ બનાવો. **07**



Fig A

Ge.1 30 MVA 10.5 KV $X'' = 1.6 \text{ ohm}$
 Ge.2 15 MVA 6.6 KV $X'' = 1.2 \text{ ohm}$
 Ge.3 25 MVA 6.6 KV $X'' = 0.56 \text{ ohm}$
 T1 15 MVA 33/11 KV $X = 15.2 \text{ ohm per ph on H.T. side}$
 T2 15 MVA 33/6.2 KV $X = 16 \text{ ohm per ph on H.T. side}$
 ટ્રાન્સમિશન લાઈન 20.5 ohm per ph

- બ નીચેનું સિંગલ ફેસ representation આપો.
 i) Y-Y 3 ફેસ ટ્રાન્સફોર્મર
 ii) Y-Delta 3 ફેસ ટ્રાન્સફોર્મર

07

- પ્રશ્ન-૨** અ PQ અને PV બસ માટે લોડ ફલો સોલ્યુશન મેળવવા ગોસ સિડલ પદ્ધતિ સમજાવો. **07**
 બ PQ બસ માટે લોડ ફલો સોલ્યુશન માટે ન્યુટન રાપસન અલગોરિધમ લખો. **07**

અથવા

- બ લોડ ફલો સોલ્યુશન મેળવવા માટે ફાસ્ટ ડિકપલ્ડ લોડ ફલો પદ્ધતિ અને N-R પદ્ધતિ સરખાવો. **07**

પ્રશ્ન-૩

- અ ઇકોનોમિકલ ઓપરેશન માટે ટૉબો જનરેટર લોડ કરવાની પદ્ધતિ કઈ કઈ છે? **07**
 બ બે જનરેટરનું ઇકોનોમિકલ લોડીંગ ઇકવલ ઇન્ક્રિમેન્ટલ કોસ્ટ હોય તો એનું સમિકરણ શોધો, લોસીસ નીગલેટ કરો. **07**

અથવા

પ્રશ્ન-૩

- અ યુનિટ કમિટમેન્ટ એટલે શું? યુનિટ કમિટમેન્ટના constraint કયા કયા છે? **07**
 બ ફોરવર્ડ ડાયનેમિક પ્રોગ્રામિંગ ના ઉપયોગથી ? યુનિટ કમિટમેન્ટનો ફલો ચાર્ટ બનાવો. **07**

પ્રશ્ન-૪

- અ સિંગલ એરિયા અને મલ્ટિ એરિયા લોડ ફ્રિકવન્સી નો તફાવત લખો. **07**
 બ બસ એડમિટન્સ મેટ્રિક્સનો (Y BUS) બસ ઇમ્પિડન્સ મેટ્રિક્સ (Z BUS) ઉપર લાભ જણાવો. **07**

અથવા

પ્રશ્ન-૪

- અ ઓટોમેટિક વોલ્ટેજ કન્ટ્રોલ એ લોડ ફ્રિકવન્સી કન્ટ્રોલ કરતા કઈ રીતે અલગ છે? **07**

બ આકૃતિ B પરથી પાવર સિસ્ટમ નો ઝીરો સિક્વન્સ નેટવર્ક બનાવો.

07



Fig B

પ્રશ્ન-૫

અ સિંક્રોનસ મશીન માટે સાબિત કરો કે $M(pu) = \frac{H}{180f} S^2/\text{Elect. Degree}$

07

બ ઈકવલ એરિયા ક્રાઈટેરિયન પદ સમજાવો.

07

અથવા

પ્રશ્ન-૫

અ ટ્રાન્ઝન્ટ સ્ટેબિલિટીને અસર કરતા પરિબળો સમજાવો.

07

બ ટ્રાન્ઝન્ટ સ્ટેબિલિટીને મેઈન્ટેન કરવાની નવિ પધ્ધતિ સમજાવો.

07
